

# Simon Fraser University

## Mechatronic Systems Engineering

### Final Exam for ENSC 226: Electronic Circuits

Instructor: Behraad Bahreyni

16 April 2012

Time: 150 minutes

Name: \_\_\_\_\_

Student number: \_\_\_\_\_

To verify identity, each candidate should be prepared to produce, upon request, his/her Simon Fraser University Library/IO card.

All writing must be submitted with this examination booklet (notes, drafts, calculations, etc.). This booklet must not be torn or mutilated in any way, and must not be taken from the examination room.

**Caution:** In accordance with the University's Academic Honesty Policy (T10.02), academic dishonesty in any form will not be tolerated. Prohibited acts include, but are not limited to, the following:

- making use of any books, papers, electronic devices or memoranda, other than those authorized by the examiners;
- speaking or communicating with other students who are writing examinations;
- copying from the work of other candidates;
- purposely exposing written papers to the view of other candidates.

| Question     | Mark |
|--------------|------|
| 1            | / 10 |
| 2            | / 15 |
| 3            | / 20 |
| 4            | / 20 |
| 5            | / 20 |
| 6            | / 10 |
| 7            | / 15 |
| <b>Total</b> | /110 |



Name: \_\_\_\_\_

Student number: \_\_\_\_\_

Final exam

Time: 150 minutes

April 16, 2012

Page: 2/14

Physical model of a diode:  $I_D = I_s \left( e^{\frac{V_D}{V_T}} - 1 \right)$ **For BJTs:**

|     | Active  | Saturation                                     | Cut-off                                 |
|-----|---|--|---|
|     | BE forward biased<br>BC reverse biased              | BE forward biased<br>BC forward biased         | BE reverse biased<br>BC reverse biased  |
| npn | $I_C = \beta I_B = \alpha I_E, V_{BE} \approx 0.7V$ | $I_B > \frac{I_C}{\beta}, V_{CE} \approx 0.2V$ | $I_B \approx I_C \approx I_E \approx 0$ |
| pnp | $I_C = \beta I_B = \alpha I_E, V_{EB} \approx 0.7V$ | $I_B > \frac{I_C}{\beta}, V_{EC} \approx 0.2V$ | $I_B \approx I_C \approx I_E \approx 0$ |

$$I_C(\text{active}) = I_s e^{\frac{|V_{BE}|}{V_T}} \left( 1 + \frac{|V_{CE}|}{V_A} \right)$$


$$\alpha = \frac{\beta}{\beta + 1}$$

$$V_T = 25mV$$

$$g_m = \frac{1}{r_m} = \frac{I_C}{V_T}$$

$$r_\pi = \beta r_m = \frac{\beta}{g_m}$$

$$r_o = \frac{V_A}{I_C}$$

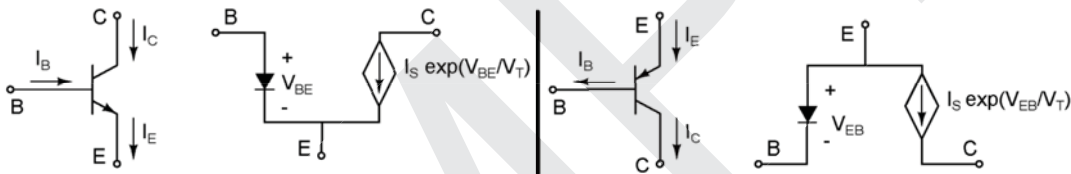**For MOSFETs:**

|                          | Saturation                                    | Triode  | Cut-off                                       |
|--------------------------|---|---|---|
| NFET<br>( $V_{TH} > 0$ ) | $V_{GS} > V_{TH} \text{ \& } V_{GD} < V_{TH}$ | $V_{GS} > V_{TH} \text{ \& } V_{GD} > V_{TH}$ | $V_{GS} < V_{TH} \text{ \& } V_{GD} < V_{TH}$ |
| PFET<br>( $V_{TH} < 0$ ) | $V_{GS} < V_{TH} \text{ \& } V_{GD} > V_{TH}$ | $V_{GS} < V_{TH} \text{ \& } V_{GD} < V_{TH}$ | $V_{GS} > V_{TH} \text{ \& } V_{GD} > V_{TH}$ |

$$I_D(\text{saturation}) = \frac{K'}{2} (V_{GS} - V_{TH})^2 (1 + \lambda V_{DS})$$

$$K' \equiv K_n = \mu_n C_{ox} \frac{W}{L} \text{ for NFETS}$$


$$K' \equiv K_p = \mu_p C_{ox} \frac{W}{L} \text{ for PFETS}$$

$$I_D(\text{triode}) = \frac{K'}{2} [2(V_{GS} - V_{TH})V_{DS} - V_{DS}^2]$$

$$r_{DS}(\text{deep triode}) \approx \frac{1}{K'(V_{GS} - V_{TH})}$$

$$g_m = K'(V_{GS} - V_{TH}) = \sqrt{2K'I_D} = \frac{2I_D}{V_{GS} - V_{TH}}$$

$$r_o = \frac{1}{\lambda I_D}$$

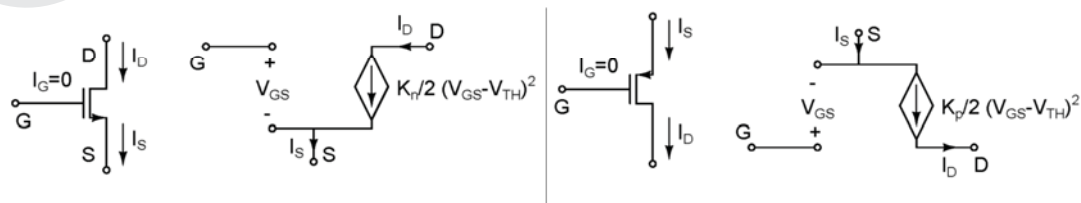

Name: \_\_\_\_\_


Student number: \_\_\_\_\_

Final exam


Time: 150 minutes

April 16, 2012


Page: 3/14

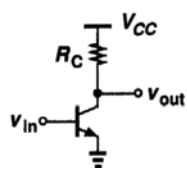


$$A_v = -g_m(R_C \parallel r_O)$$

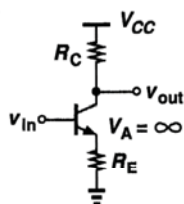

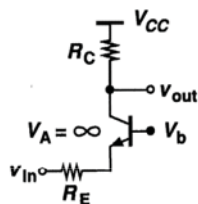
$$A_v = -\frac{R_C}{\frac{1}{g_m} + R_E}$$



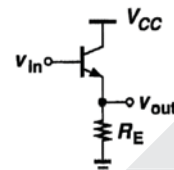
$$A_v = \frac{R_C}{\frac{1}{g_m} + R_E}$$



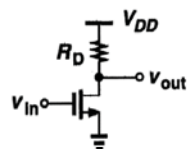
$$A_v = \frac{R_E \parallel r_O}{\frac{1}{g_m} + R_E \parallel r_O}$$




$$A_v = -g_m(R_D \parallel r_O)$$

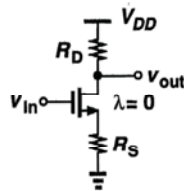









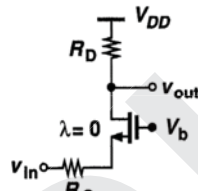
$$A_v = -\frac{R_D}{\frac{1}{g_m} + R_S}$$


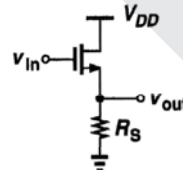
$$A_v = \frac{R_D}{\frac{1}{g_m} + R_S}$$


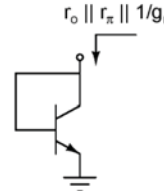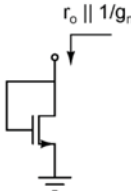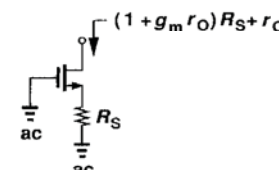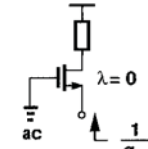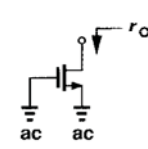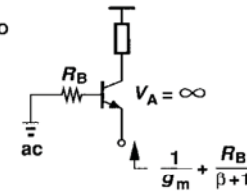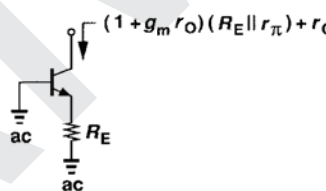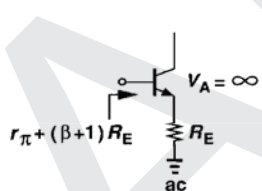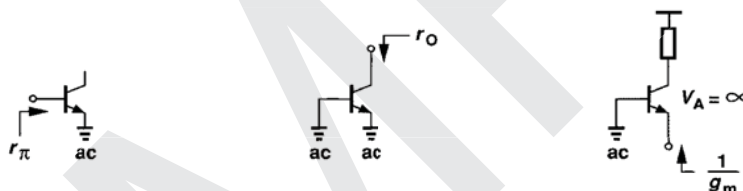
$$A_v = \frac{R_S \parallel r_O}{\frac{1}{g_m} + R_S \parallel r_O}$$



Name: \_\_\_\_\_

Student number: \_\_\_\_\_

Final exam


Time: 150 minutes

April 16, 2012

Page: 4/14

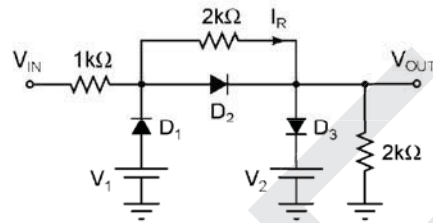**Question 1** [10 marks]

Consider the diode circuit to the right where the diodes are **ideal**,  $V_1 = -5V$ , and  $V_2 = +2V$ . The input voltage is slowly increased from  $-10V$  to  $+10V$ .



**1.a.** [5 marks] What is the range for  $I_R$ ?

\_\_\_\_\_  $< I_R <$  \_\_\_\_\_

**1.b.** [5 marks] Diode  $D_1$  turns off as the input voltage is increased from  $-10V$ . What is the minimum input voltage that switches diode  $D_1$  off?

Name: \_\_\_\_\_

Student number: \_\_\_\_\_

Final exam


Time: 150 minutes

April 16, 2012

Page: 5/14

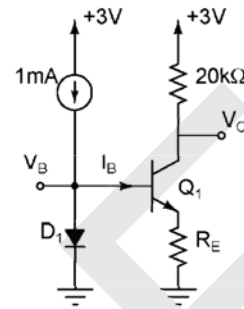**Question 2** [15 marks]

Consider the circuit to the right where the base current of  $Q_1$  can be ignored (i.e.,  $I_B \approx 0$  or  $\beta \rightarrow \infty$ ). For both the transistor and the diode, assume  $V_T = 25\text{mV}$ ,  $I_S = 10^{-15}\text{A}$ , and  $V_A = \infty$ . Provide the answers with three significant digits.



2.a. [5 marks] What is  $V_B$ ?

$V_B = \underline{\hspace{2cm}}\text{V}$

2.b. [7 marks] If  $R_E = 1\text{k}\Omega$ , what is the collector current of  $Q_1$  (Hint: use iterations)?

$I_C = \underline{\hspace{2cm}}\text{mA}$

2.c. [3 marks] What is  $V_C$  for the collector current calculated in the above?

$V_C = \underline{\hspace{2cm}}\text{V}$

Name: \_\_\_\_\_

Student number: \_\_\_\_\_

Final exam

Time: 150 minutes

April 16, 2012

Page: 6/14


**Question 3** [20 marks]

Consider the circuit shown to the right where the capacitors are assumed to be AC short circuits. Assume  $\beta = 100$ ,  $V_T = 25mV$ ,  $V_{EB}(on) = 0.6V$ ,  $V_{EC}(sat) = 0.2V$ , and  $|V_A| = \infty$ .

**3.a.** [4 marks] If  $R_C = 10k\Omega$ , what is the collector current of the transistor? Verify the operating region of the transistor.

 $I_C = \text{_____} mA$ 

Operating region: \_\_\_\_\_

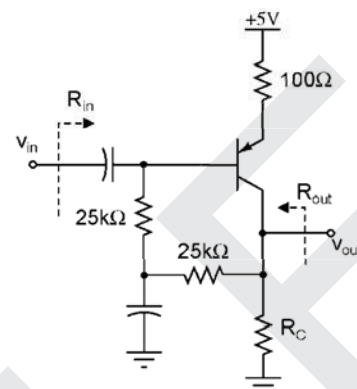

**3.b.** [4 marks] Calculate the small signal parameters and draw the small signal equivalent circuit.

 $g_m = \text{_____} mS$  $r_\pi = \text{_____} k\Omega$

Name: \_\_\_\_\_

Student number: \_\_\_\_\_

Final exam

Time: 150 minutes

April 16, 2012

Page: 7/14

3.c. [4 marks] What is the voltage gain of the circuit?

$$A_v = \frac{v_{out}}{v_{in}} = \underline{\hspace{2cm}} V/V$$

3.d. [4 marks] What is the input resistance of the circuit?

$$R_{in} = \underline{\hspace{2cm}} k\Omega$$

3.e. [4 marks] What is the output resistance of the circuit?

$$R_{out} = \underline{\hspace{2cm}} k\Omega$$

Name: \_\_\_\_\_

Student number: \_\_\_\_\_

Final exam

Time: 150 minutes

April 16, 2012

Page: 8/14


**Question 4** [20 marks]

Consider the circuit shown to the right where the capacitor is AC short circuit. Assume  $R_S = 15k\Omega$ ,  $V_{TH} = 2V$ ,  $K_n = 1mA/V^2$ , and  $\lambda = 0$ .

**4.a.** [6 marks] What is the drain current of the transistor? Verify the operating region of the transistor.

$I_D = \text{_____} mA$

Operating region: \_\_\_\_\_

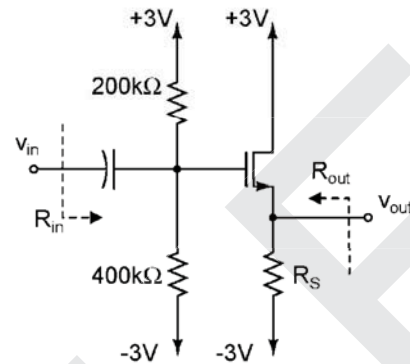

**4.b.** [3 marks] Calculate  $g_m$  and draw the small signal equivalent circuit.

$g_m = \text{_____} mS$



Name: \_\_\_\_\_

Student number: \_\_\_\_\_

Final exam

Time: 150 minutes

April 16, 2012

Page: 9/14

**4.c.** [4 marks] What is the voltage gain of the circuit?

$$A_v = \frac{v_{out}}{v_{in}} = \underline{\hspace{2cm}} \text{ V/V}$$

**4.d.** [3 marks] What is the input resistance of the circuit?

$$R_{in} = \underline{\hspace{2cm}} \text{ k}\Omega$$

**4.e.** [4 marks] What is the output resistance of the circuit?

$$R_{out} = \underline{\hspace{2cm}} \text{ k}\Omega$$

Name: \_\_\_\_\_

Student number: \_\_\_\_\_

Final exam Time: 150 minutes


April 16, 2012

Page: 10/14

**Question 5** [20 marks]

The OpAmps are ideal in circuits shown below.

5.a. [5 marks] What is the input resistance of the circuit as a function of resistor values?

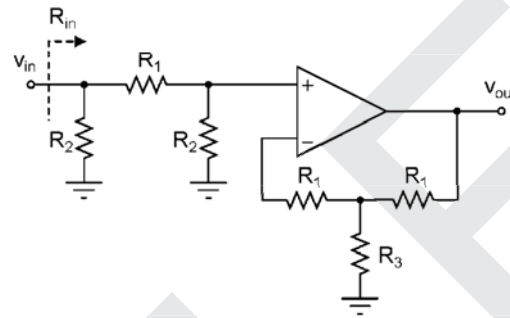 $R_{in} =$  \_\_\_\_\_


5.b. [5 marks] What is the voltage gain of the circuit assuming  $R_1 = 2k\Omega$ ,  $R_2 = 10k\Omega$ , and  $R_3 = 100\Omega$ ?

 $A_v = \frac{v_{out}}{v_{in}} =$  \_\_\_\_\_ V/V

Name: \_\_\_\_\_

Student number: \_\_\_\_\_


Final exam

Time: 150 minutes

April 16, 2012

Page: 11/14

5.c. [4 marks] What is the input resistance of the circuit as a function of resistor values?

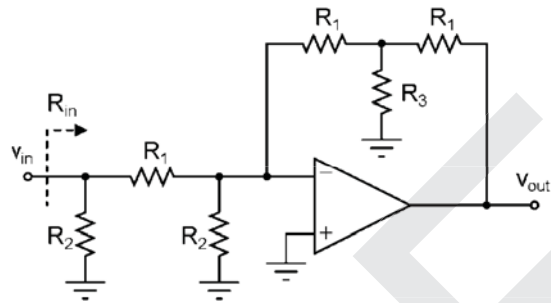 $R_{in} =$  \_\_\_\_\_

5.d. [6 marks] What is the voltage gain of the circuit assuming  $R_1 = 2k\Omega$ ,  $R_2 = 10k\Omega$ , and  $R_3 = 100\Omega$ ?

 $A_v = \frac{v_{out}}{v_{in}} =$  \_\_\_\_\_ V/V

Name: \_\_\_\_\_

Student number: \_\_\_\_\_

Final exam

Time: 150 minutes


April 16, 2012

Page: 12/14

**Question 6** [10 marks]

Shown to the right is a common-collector circuit similar to what you studied in Lab 3.

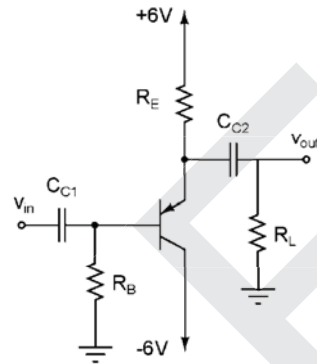**6.a.** [4 marks] We monitor the output signal while applying a signal with a constant amplitude to the input of the circuit. We notice that the amplifier gain at 1kHz is smaller than the gain at 100kHz. The gain remains relatively constant for frequencies higher than 100kHz. Explain what may be the most possible reason for this observation.



**6.b.** [6 marks] We measure the gain of the amplifier at 1MHz with  $R_L = 100\Omega$  to be 0.9V/V. When we change the load resistance to  $R_L = 200\Omega$ , the gain increases to 0.95V/V. What is the output resistance of the circuit? (Hint: you do not need device parameters or component values.)

Name: \_\_\_\_\_

Student number: \_\_\_\_\_

Final exam

Time: 150 minutes

April 16, 2012

Page: 13/14

**Question 7** [15 marks]

The OpAmp is ideal in circuit shown to the right.


The transistor parameters are  $\beta = 100$ ,  $V_T = 25mV$ ,  $V_{BE(on)} = 0.6V$ , and  $V_{CE(sat)} = 0.2V$ . Assume  $R_1 = 35k\Omega$ ,  $R_2 = 1k\Omega$ , and  $R_3 = 1M\Omega$ .

$V_{DC}$  is a  $100mV$  DC voltage source and  $v_{ac}$  is a small signal AC voltage source.

7.a. [4 marks] What are the DC collector current and voltage of the transistor?

$I_C = \underline{\hspace{2cm}} mA$

$V_C = \underline{\hspace{2cm}} V$

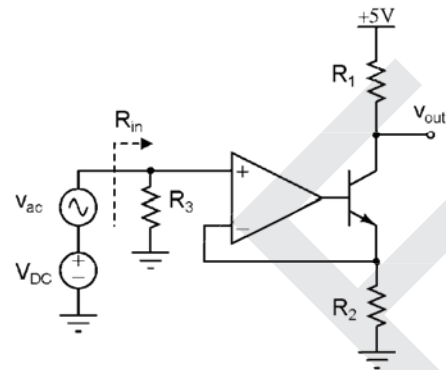

7.b. [7 marks] What is the small signal voltage gain of the circuit?

$A_v = \frac{v_{out}}{v_{ac}} = \underline{\hspace{2cm}} V/V$

7.c. [4 marks] What is the input resistance of the circuit?

$R_{in} = \underline{\hspace{2cm}}$

Name: \_\_\_\_\_

Student number: \_\_\_\_\_

Final exam

Time: 150 minutes

April 16, 2012

Page: 14/14

**You may use this space to answer any of the questions with proper reference to the question.**

SAMPLE