

Simon Fraser University

Mechatronic Systems Engineering

Final Exam for ENSC 226: Electronic Circuits

Instructor: Behraad Bahreyni

13 April 2011

Time: 150 minutes

Name: Solutions

Student number: _____

To verify identity, each candidate should be prepared to produce, upon request, his/her Simon Fraser University Library/IO card.

All writing must be submitted with this examination booklet (notes, drafts, calculations, etc.). This booklet must not be torn or mutilated in any way, and must not be taken from the examination room.

Caution: In accordance with the University's Academic Honesty Policy (T10.02), academic dishonesty in any form will not be tolerated. Prohibited acts include, but are not limited to, the following:

- making use of any books, papers, electronic devices or memoranda, other than those authorized by the examiners;
- speaking or communicating with other students who are writing examinations;
- copying from the work of other candidates;
- purposely exposing written papers to the view of other candidates.



Question	Mark
1	/ 40
2	/ 15
3	/ 20
4	/ 15
5	/ 10
Total	/100

Name: _____

Student number: _____

Final exam

Time: 150 minutes

April 13, 2011

Page: 2/14

Physical model of a diode: $I_D = I_S \left(e^{\frac{V_D}{V_T}} - 1 \right)$

For BJTs:

	Active	Saturation	Cut-off
	BE forward biased BC reverse biased	BE forward biased BC forward biased	BE reverse biased BC reverse biased
npn	$I_C = \beta I_B = \alpha I_E, V_{BE} \approx 0.7V$	$I_B > \frac{I_C}{\beta}, V_{CE} \approx 0.2V$	$I_B \approx I_C \approx I_E \approx 0$
pnp	$I_C = \beta I_B = \alpha I_E, V_{EB} \approx 0.7V$	$I_B > \frac{I_C}{\beta}, V_{EC} \approx 0.2V$	$I_B \approx I_C \approx I_E \approx 0$

$$I_C(\text{active}) = I_S e^{\frac{|V_{BE}|}{V_T}} \left(1 + \frac{|V_{CE}|}{V_A} \right)$$


$$\alpha = \frac{\beta}{\beta + 1}$$

$$V_T = 25mV$$

$$g_m = \frac{1}{r_m} = \frac{I_C}{V_T}$$

$$r_\pi = \beta r_m = \frac{\beta}{g_m}$$

$$r_o = \frac{V_A}{I_C}$$

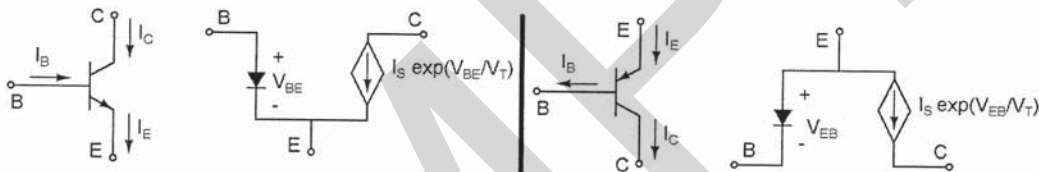

For MOSFETs:

	Saturation	Triode	Cut-off
NFET ($V_{TH} > 0$)	$V_{GS} > V_{TH} \text{ \& } V_{GD} < V_{TH}$	$V_{GS} > V_{TH} \text{ \& } V_{GD} > V_{TH}$	$V_{GS} < V_{TH} \text{ \& } V_{GD} < V_{TH}$
PFET ($V_{TH} < 0$)	$V_{GS} < V_{TH} \text{ \& } V_{GD} > V_{TH}$	$V_{GS} < V_{TH} \text{ \& } V_{GD} < V_{TH}$	$V_{GS} > V_{TH} \text{ \& } V_{GD} > V_{TH}$

$$I_D(\text{saturation}) = \frac{K'}{2} (V_{GS} - V_{TH})^2 (1 + \lambda V_{DS})$$

$$K' \equiv \mu_n C_{ox} \frac{W}{L} \text{ for NFETS}$$


$$K' \equiv \mu_p C_{ox} \frac{W}{L} \text{ for PFETS}$$

$$I_D(\text{triode}) = \frac{K'}{2} [2(V_{GS} - V_{TH})V_{DS} - V_{DS}^2]$$

$$r_{DS}(\text{triode}) \approx \frac{1}{K'(V_{GS} - V_{TH})}$$

$$g_m = K'(V_{GS} - V_{TH}) = \sqrt{2K'I_D} = \frac{2I_D}{V_{GS} - V_{TH}}$$

$$r_o = \frac{1}{\lambda I_D}$$

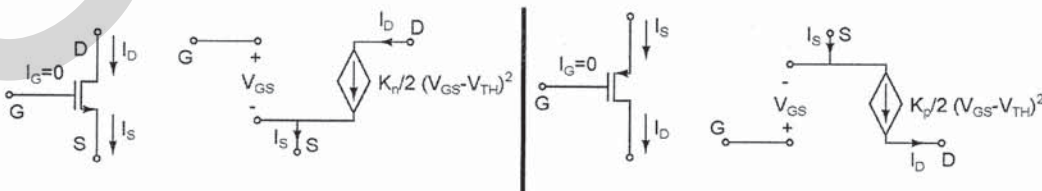

Name: _____


Student number: _____

Final exam


Time: 150 minutes

April 13, 2011


Page: 3/14

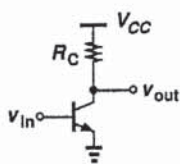


$$A_v = -g_m(R_C \parallel r_o)$$

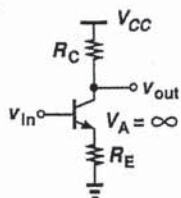

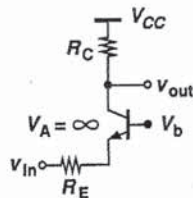
$$A_v = -\frac{R_C}{\frac{1}{g_m} + R_E}$$



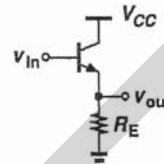
$$A_v = \frac{R_C}{\frac{1}{g_m} + R_E}$$



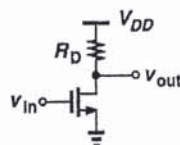
$$A_v = \frac{R_E \parallel r_o}{\frac{1}{g_m} + R_E \parallel r_o}$$




$$A_v = -g_m(R_D \parallel r_o)$$

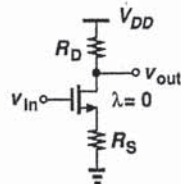











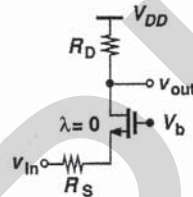
$$A_v = -\frac{R_D}{\frac{1}{g_m} + R_S}$$


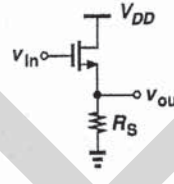
$$A_v = \frac{R_D}{\frac{1}{g_m} + R_S}$$


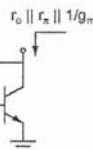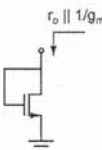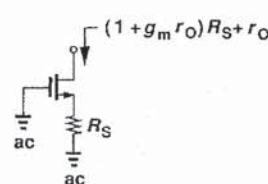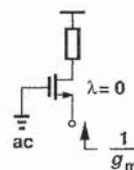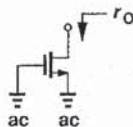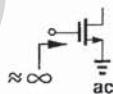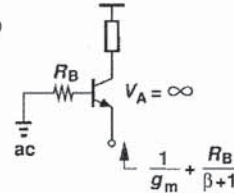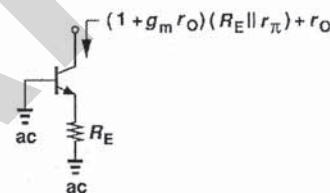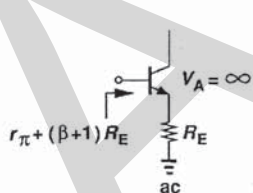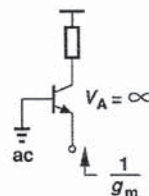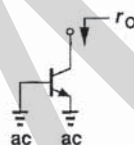
$$A_v = \frac{R_S \parallel r_o}{\frac{1}{g_m} + R_S \parallel r_o}$$



Name: _____

Student number: _____

Final exam

Time: 150 minutes

April 13, 2011


Page: 4/14

Question 1. [40 marks]

Circle the correct answer for each of the following problems.

1.a. [5 marks] What is the range for the output voltage if $-36V < v_{in} < +36V$? Assume the diodes are ideal.

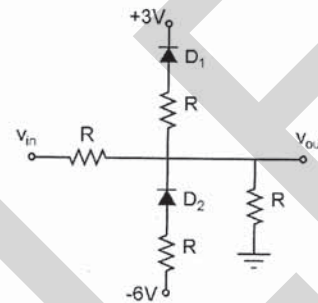- (a) $-12V < v_{out} < +12V$ (b) $-10V < v_{out} < +9V$
 (c) $-14V < v_{out} < +13V$ (d) $-18V < v_{out} < +18V$
 (e) None of the above



$$v_{out} = \frac{v_{in}}{3} + 1 \quad \text{for large } v_{in}$$

$$v_{out} = \frac{v_{in}}{3} - 2 \quad \text{for small } v_{in}$$

1.b. [5 marks] A student wants to measure the input resistance of an amplifier using the method you learned in Lab 4. However, he only has a fixed $10k\Omega$ resistor instead of a proper variable resistor. When he puts this resistor in series with the input of the amplifier, the output signal amplitude changes from 1V to 0.80V. What is the input resistance of this amplifier?

- (a) $10k\Omega$
 (b) $20k\Omega$
 (c) $30k\Omega$
 (d) $40k\Omega$
 (e) None of the above

(b) $20k\Omega$ (d) $40k\Omega$

+5



+2 for the model

$$\frac{R_{in}}{10k + R_{in}} = 0.8 \rightarrow 0.2 R_{in} = 8k\Omega$$

$$\rightarrow R_{in} = 40k\Omega$$

Name: _____

Student number: _____

Final exam

Time: 150 minutes

April 13, 2011

Page: 5/14

I.c. [5 marks] Assume $V_A = \infty$, $\beta = \infty$ (i.e., ignore the base current) and $R_C = 2.4k\Omega$. What should the value of I_S be such that the base-collector junction is forward biased by 100mV?


(a) $4.83 \times 10^{-15} A$

(b) $1.27 \times 10^{-17} A$

(c) $3.76 \times 10^{-14} A$

(d) $8.03 \times 10^{-12} A$

(e) None of the above

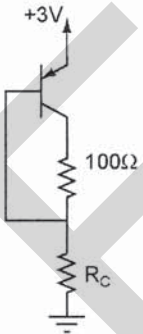


$$I_C = 1mA \quad (+2)$$

$$3 = 0.025 \ln \frac{1mA}{I_S} + 2.4k \times 1mA$$

$$\Rightarrow I_S = 3.775 \times 10^{-14} A$$

I.d. [5 marks] Assume the circuit is properly biased to keep the transistor in active region and $V_A < \infty$ (i.e., take Early effect into account). Using formulas provided on page 3, find out the input resistance, R_{in} , of this circuit.

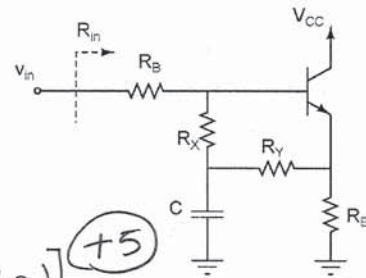The capacitor is short-circuit for small-signal analysis.



$$R_{in} = R_B + R_X \parallel [r_\pi + (\beta + 1)(R_E \parallel R_Y \parallel r_o)] \quad (+5)$$

$+3$ if r_o is omitted

Name: _____

Student number: _____


Final exam

Time: 150 minutes

April 13, 2011

Page: 6/14

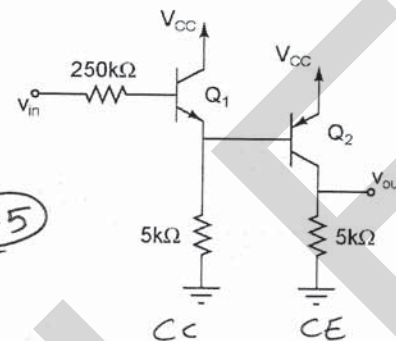I.e. [5 marks] Assume the circuit is properly biased to keep the transistors in active region and $\beta = 200$, $V_A = \infty$, and $I_{C1} = I_{C2} = 1\text{mA}$. Use formulas on page 3 to find the voltage gain, $A_v = \frac{v_{out}}{v_{in}}$, of this circuit.



(a) $A_v = 132\text{ V/V}$

(b) $A_v = -132\text{ V/V}$

+5


(c) $A_v = 198\text{ V/V}$

(d) $A_v = -198\text{ V/V}$

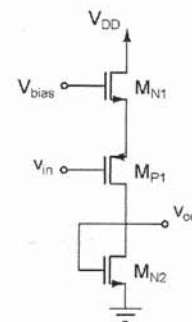(e) None of the above

+2 if (a) is selected

I.f. [5 marks] Assume the circuit is properly biased to keep the transistors in active region and that the transconductance of the PMOSFETs is twice as big as that of the NMOSFETs; i.e., $g_{mn1} = g_{mn2} = 0.5 g_{mp}$. Using formulas on page 3, find the voltage gain, $A_v = \frac{v_{out}}{v_{in}}$, of the circuit.



+5 (a) $A_v = -2/3$

(b) $A_v = +2/3$

+2

(c) $A_v = -1/3$

(d) $A_v = +1/3$

(e) None of the above

$$A_v = \frac{-1/g_{mn}}{1/g_{mp} + 1/g_{mn}} = \frac{-1}{+1 + 0.5}$$

+2 for right formula & negative answer

Name: _____

Student number: _____

Final exam

Time: 150 minutes


April 13, 2011

Page: 7/14

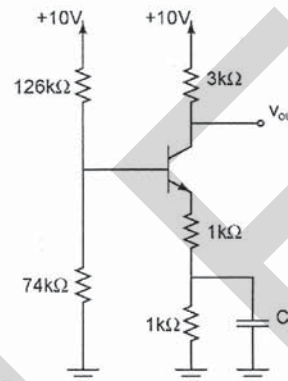1.g. [5 marks] Assume $V_A = \infty$, $V_{BE,on} = 0.7V$, $V_{CE,sat} = 0.2V$, and $\beta = \infty$ (i.e., ignore the base current). What is the maximum symmetric swing at the output? In other words, what is the peak-to-peak value of the largest output signal without distortion?

Maximum symmetric swing = 4.6V V (+1)

What limits the swing, cut-off or saturation? Saturation (+2)



$$I_{CQ} = 1.5mA$$

$$V_{CQ} = 5.5$$

$$\min V_C = 3.2$$

$$\max V_C = 10$$

$$\rightarrow \Delta V_{C,max} = 2.3V \rightarrow P_{K-PK swing} = 4.6V$$

Saturation

+1 for 4.12

1.h. [5 marks] We know that the threshold voltage of the transistor shown here is less than $2.5V$. Assume that $R_L = 100\Omega$ and $V_{in} = 100mV$. For $V_G = 3V$, $v_{out} = 80mV$ and for $V_G = 4V$, $v_{out} = 90mV$. What is the threshold voltage of this transistor?

(a) 2.0V


(c) 2.1V

(e) None of the above

(b) 2.2V

(d) 2.3V

+5

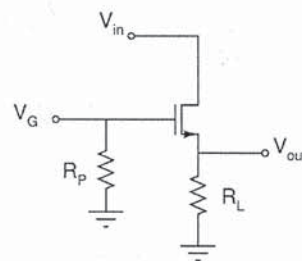

$$\left. \begin{aligned} r_{DS1} &= 100 \left(\frac{100}{80} - 1 \right) = 25\Omega \\ r_{DS2} &= 100 \left(\frac{100}{90} - 1 \right) = \frac{100}{9}\Omega \end{aligned} \right\} \rightarrow \frac{r_{DS1}}{r_{DS2}} = \frac{25 \times 9}{100} = \frac{4 - V_{TH}}{3 - V_{TH}}$$

$$\rightarrow 27 - 9V_{TH} = 16 - 4V_{TH} \Rightarrow V_{TH} = \frac{11}{5} = 2.2V$$

Name: _____

Student number: _____

Final exam

Time: 150 minutes


April 13, 2011

Page: 8/14

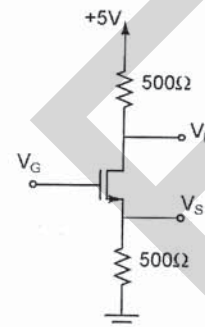Question 2. [15 marks]

For the transistor shown in the circuit to the right, $K_n = 50 \text{ mA/V}^2$, $\lambda = 0$, and $V_{TH} = 1 \text{ V}$. We slowly change V_G from 0 to +5V.

At what gate voltages does the operating region of the transistor change from one to the other?



Cut-off:

$$0 < V_G < 1 \quad (+2)$$

Saturation:

$$1 < V_G < 3.7$$

Triode:

$$3.7 < V_G < 5 \quad (+1)$$

$$V_D = V_G - V_{TH} = V_{DD} - I_D R_D \quad (+3)$$

$$V_G = V_{GS} + I_D R_D \quad (+3)$$

$$5 - 500 I_D = V_{GS} + 500 I_D - 1 \quad (+3)$$

$$\Rightarrow \begin{cases} V_{GS} = 1.43 \quad \checkmark \\ V_{GS} = 0.53 \end{cases}$$

$$I_D = 4.63 \text{ mA} \rightarrow V_{GS} = 3.714 \text{ V} \quad (+3)$$

Name: _____

Student number: _____

Final exam

Time: 150 minutes

April 13, 2011


Page: 9/14

Question 3. [20 marks]

Consider the circuit shown to the right.

For the BJT, $\beta = 100$, $V_A = \infty$, $V_{BE,on} = 0.7V$, $V_{CE,sat} = 0.2V$, and $V_A = \infty$.For the MOSFET, $K_n = 100 \text{ mA/V}^2$, $\lambda = 0$,and $V_{TH} = 1V$.

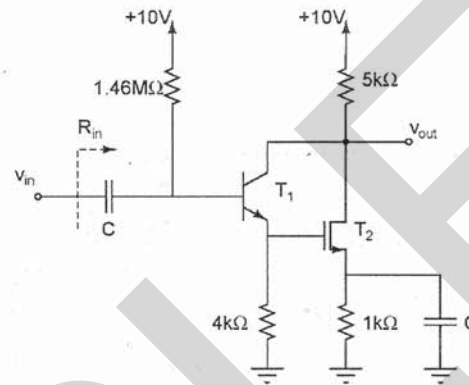Capacitors are assumed AC short circuits.



3.a. [8 marks] Calculate the operating point parameters of both transistors.

$$I_C = \underline{0.5} \text{ mA}$$

$$I_D = \underline{0.87} \text{ mA}$$

$$V_{CE} = \underline{1.15} \text{ V}$$

$$V_{DS} = \underline{2.26} \text{ V}$$

$$I_C = 0.5 \text{ mA} \quad (+3)$$

$$I_D = 0.87 \text{ mA}, V_{GS} = 1.132 \quad (+3)$$

$$V_{CE1} = 1.15 \text{ V} \quad (+1)$$

$$V_{DS2} = 2.26 \text{ V} \quad (+1)$$

Name: _____

Student number: _____


Final exam

Time: 150 minutes

April 13, 2011

Page: 10/14

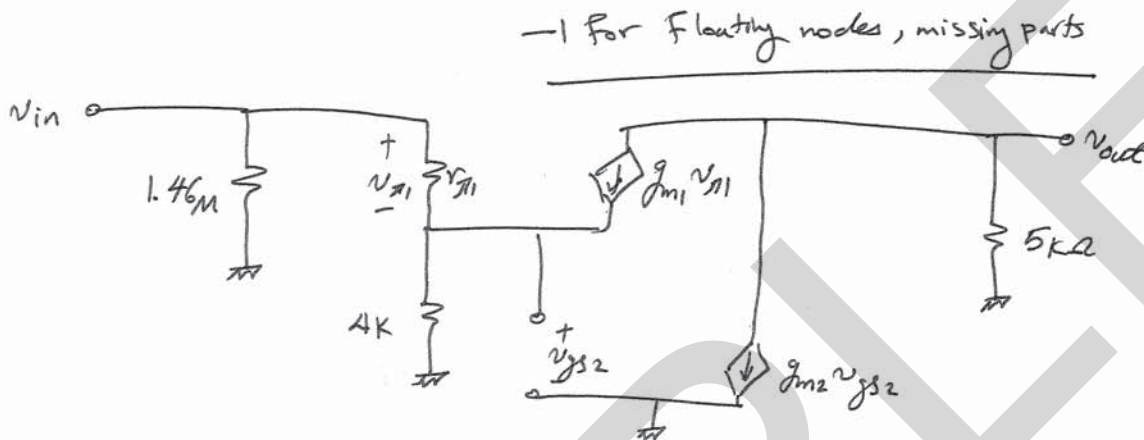3.b. [4 marks] Draw the small signal model of the circuit.



3.c. [8 marks] Use the small signal model to calculate the voltage gain of the circuit.

$$A_v = \frac{v_{out}}{v_{in}} = \underline{-66.3} \text{ V/V}$$

$$v_{in} = v_{gs1} + v_{gs2}$$

$$v_{out} = -(g_{m1} v_{gs1} + g_{m2} v_{gs2}) R_D \quad (+2)$$

$$v_{gs2} = \left(\frac{v_{gs1}}{r_{d1}} + g_{m1} v_{gs1} \right) \times 4k\Omega$$

$$v_{in} = 81.8 v_{gs1} = \frac{81.8}{81.8} v_{gs2}$$

 v_{gs2}

$$\rightarrow A_v = -66.3 \quad (+4)$$

Name: _____

Student number: _____

Final exam

Time: 150 minutes

April 13, 2011


Page: 11/14

Question 4. [15 marks]

Assume the OpAmp in circuit shown here is ideal.

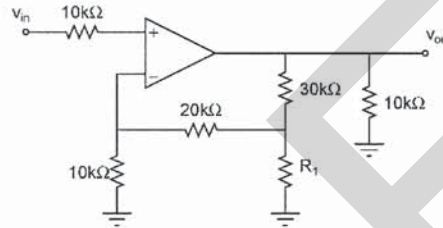3.a. [10 marks] What is the voltage gain of the circuit if $R_1 = 2k\Omega$.

$$A_v = \frac{v_{out}}{v_{in}} = \underline{+51} \text{ V/V}$$



$$\frac{v_x}{R_1} + \frac{v_x - v^-}{20k} + \frac{v_x - v_o}{30k} = 0 \quad (+2)$$

$$\frac{v_x - v^-}{20k} = \frac{v^-}{110k} \quad (+2)$$

Ignoring 10k at v^+ & $v_o \rightarrow (+4)$

$$R_1 = 2k\Omega = +51 \quad (+2)$$

3.b. [5 marks] What is the voltage gain of the circuit if $R_1 \rightarrow \infty$.

$$A_v = \frac{v_{out}}{v_{in}} = \underline{+6} \text{ V/V}$$

$$R_1 \rightarrow \infty \rightarrow A_v = +6 \text{ V/V} \quad (+5)$$

Name: _____

Student number: _____

Final exam


Time: 150 minutes

April 13, 2011

Page: 12/14

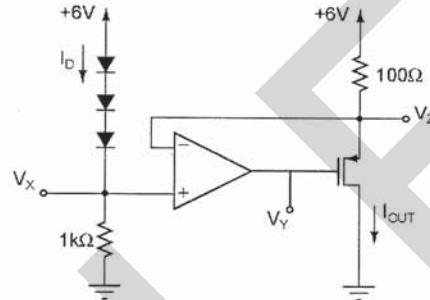Question 5. [10 marks]

Assume the OpAmp in circuit shown here is ideal.
For the MOSFET, $K_p = 200 \text{ mA/V}^2$, $\lambda = 0$, and $V_{TH} = -2\text{V}$. The diodes are identical.



5.a. [3 marks] For each diode, $I_D = I_S e^{\frac{V_D}{nV_T}}$ where $I_S = 10^{-9} \text{ A}$ and $n = 2$. What is V_X ?

$$V_X = \underline{3.8} \text{ V}$$

$$6 = 2 \times 3 \times 0.025 \ln \frac{I_D}{10^{-9}} + I_D \times 1\text{k} \quad *$$

$$I_D = 3.9 \text{ mA} \rightarrow * = 6.17$$

$$I_D = 3.8 \text{ mA} \rightarrow V_X = 3.8 \text{ V}$$

5.b. [4 marks] What is I_{OUT} ?

$$I_{OUT} = \underline{22} \text{ mA}$$

$$I_{out} = \frac{2.2}{100} = 22 \text{ mA} \quad (+2)$$

(+2)

5.c. [3 marks] What is V_Y ?

$$V_Y = \underline{1.33} \text{ V}$$

$$I_D = 0.1 (V_{GS} + 2)^2 \rightarrow V_{GS} = \begin{cases} -2.47 \text{ V} \checkmark \\ -1.53 \text{ V} \times \end{cases} \quad (+2)$$

$$V_Y - V_Z = -2.47 \text{ V} \rightarrow V_Y = 3.8 - 2.47 = 1.33 \text{ V} \quad (+2)$$

Name: _____

Student number: _____

Final exam

Time: 150 minutes

April 13, 2011

Page: 13/14

You may use this space to answer any of the questions with proper reference to the question.

SAMPLE

Name: _____

Student number: _____

Final exam

Time: 150 minutes

April 13, 2011

Page: 14/14

You may use this space to answer any of the questions with proper reference to the question.

SAMPLE