

Simon Fraser University

Mechatronic Systems Engineering

Midterm Exam for ENSC 226: Electronic Circuits

Instructor: Behraad Bahreyni

1 March 2011

Time: 110 minutes

Name: Solutions

Student number: _____

Question	Mark
1	/ 30
2	/ 20
3	/ 20
4	/ 30
Total	/100



Name: _____

Student number: _____

Midterm exam

Time: 110 minutes

March 1, 2011

Page: 3/10

Question 1. [30 marks]

Circle the correct answer for each of the following problems.

1.a. [5 marks] During lab 1, you learned that the basic equation for the physical model of diodes needed to be modified. What was the additional parameter that was introduced? How was the equation for the small signal resistance of the diode modified?

Additional parameter: n

$$r_d = \frac{nVT}{I_D}$$

1.b. [5 marks] Assume that you are given a working BJT whose model number has been erased from its package. We want to use a multimeter similar to the one you used in the lab to determine the type (npn or pnp) and pins (base, collector, and emitter) of the transistor. Using the diode more on the multimeter, the following data is obtained:

Between pins 2&1: 0.5V

Between pins 1&2: OPEN

Between pins 3&1: 0.7V

Between pins 1&3: OPEN

Between pins 2&3: OPEN

Between pins 3&2: OPEN

where, for example, the measurement between pins 1&2 is taken by connecting the positive lead of the multimeter to pin 1 and its negative lead to pin 2. What are the type and pin arrangement of this transistor?


(a) npn; pin 1: Base, pin 2: Emitter, pin 3: Collector

(b) npn; pin 1: Base, pin 2: Collector, pin 3: Emitter

(c) pnp; pin 1: Base, pin 2: Emitter, pin 3: Collector

☒ (d) pnp; pin 1: Base, pin 2: Collector, pin 3: Emitter

(e) None of the above

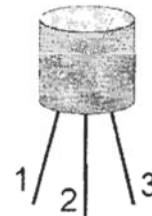

1.c. [5 marks] What is the output ripple voltage of the circuit shown below? Assume $R_L = 1k\Omega$, $C_L = 100\mu F$, $v_{in} = 5.7 \sin 2\pi 100t$ and $V_{D,on} = 0.7V$.


(a) 0.5V

(b) 0.3V

(c) 0.36V

☒ (d) 0.43V

(e) None of the above

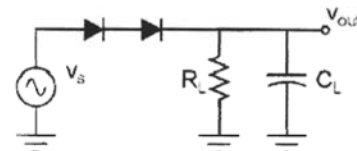

$$V_r = \frac{5.7 - 2 \times 0.7}{100 \times 10^{-6} \times 10^3} = \frac{4.3}{10} = 0.43V$$

Name: _____

Student number: _____

Midterm exam


Time: 110 minutes

March 1, 2011

Page: 4/10

1.d. [10 marks] Assume $I_{SD} = 1\text{fA}$, $I_{SQ} = 10\text{fA}$, $\beta = \infty$, and $V_A = \infty$.What is the collector current, I_C , if $R_B = 10\text{k}\Omega$?

$$I_C = \underline{4.35} \text{ mA}$$

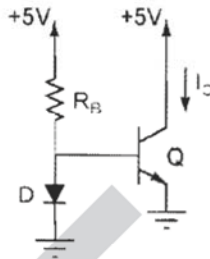

$$5 = I_D \times 10\text{k} + 0.025 \ln \frac{I_D}{10^{-15}} \quad (5)$$


$$I+① \quad I_D = \frac{5-0.7}{10\text{k}} = 430\mu\text{A} \rightarrow A = 4.96\text{V}$$

$$I_D = 350\mu\text{A} \rightarrow A = 4.16$$

$$I_D = \frac{4.96}{10\text{k}} = 496\mu\text{A} \rightarrow A = 5.02 \checkmark \rightarrow I_D = 435\mu\text{A}$$

$$\rightarrow I_C = 10 I_D = 4.35\text{mA} \quad (5)$$

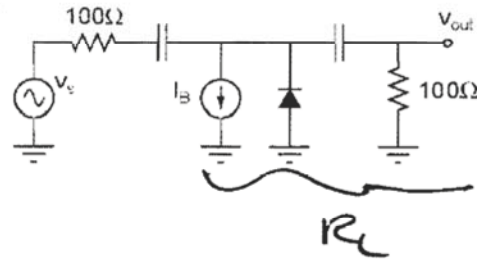1.e. [5 marks] Assume $I_B = 0.2\text{mA}$ and that the capacitors are short circuits for small signal operation. What is the small signal output voltage, v_{out} ?



$$v_{out} = v_s \times \underline{0.36} \quad (2)$$

$$r_d = \frac{V_T}{I_D} = \frac{25}{0.2} = 125\Omega \quad (3)$$

$$R_L = 100 \parallel 125 = 55.6$$

$$\rightarrow v_{out} = \frac{55.6}{155.6} v_s = 0.36 v_s$$

Name: _____

Student number: _____

Midterm exam

Time: 110 minutes


March 1, 2011

Page: 5/10

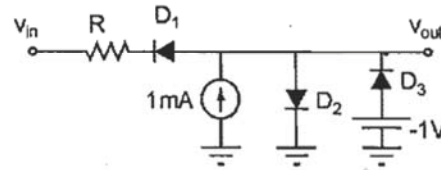Question 2. [20 marks]

Using the constant voltage drop model for the diodes, draw the input output characteristic curve for $-5V < v_{in} < +5V$ for the circuit shown.

Label all important information on your graph.



$$v_{in} \rightarrow -\infty \rightarrow D_1: \text{on}, D_3: \text{on}, D_2: \text{off}$$

$$v_{out} = -1.7V$$

D_1 turns off at $I_{D1} = 0$ X will not happen before D_2 turns on

D_3 turns off if $I_{D3} = 0$: $I_{D3} + 1mA = I_{D1}$

$$I_{D1} = \frac{-1.7 - 0.7 - v_{in}}{R} \quad I_{D3} = 0 \rightarrow \frac{-2.4 - v_{in}}{R} = 1mA \rightarrow v_{in} = -2.4 - R \times 1mA$$

$$D_1: \text{on}, D_2: \text{off}, D_3: \text{off} \rightarrow v_{out} = 0.7 + R \times 1mA + v_{in}$$

D_2 turns on if $v_{out} \leq 0.7$ or $v_{in} = -R \times 1mA$


D_1 turns off if $I_{D1} = 0$ X

$$D_1: \text{on}, D_2: \text{on}, D_3: \text{off}$$

$$v_{out} = +0.7$$

D_1 turns off if $I_{D1} = 0$ $\frac{v_{in}}{R} = 0 \rightarrow v_{in} = 0$ However, v_{out} does not change

$$R = 1k\Omega$$

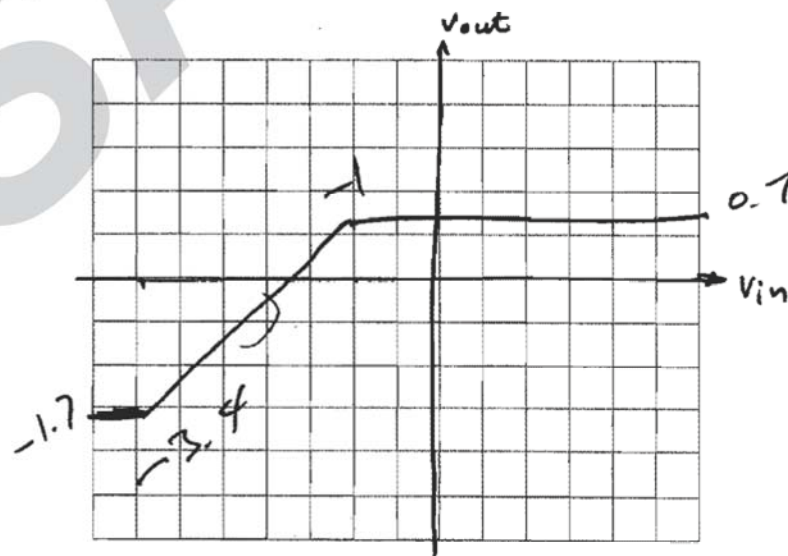

Name: _____

Student number: _____

Midterm exam

Time: 110 minutes

March 1, 2011


Page: 6/10

Question 3. [20 marks]

What are I_C and V_{EC} ? Assume $V_{CC} = +4V$, $\beta = 100$, and $V_A = \infty$. Justify any assumption you make.

$$I_C = \frac{1.33}{1.93} \text{ mA} \quad (14)$$
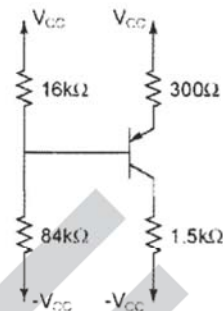
$$V_{EC} = \frac{5.6}{4.52} \text{ V} \quad (6)$$




$$I_B = 0 \rightarrow V_B = 0.84 \times 8 - 4 = 2.72 \text{ V} \quad (6)$$

$$\rightarrow V_E = 3.42 \rightarrow I_E = I_C = 1.93 \text{ mA} \rightarrow V_{EC} = 3.42$$

$$V_{EC} = 3.42 - (1.5 \times 1.93 - 4) = 4.52 \text{ V} \quad (4)$$
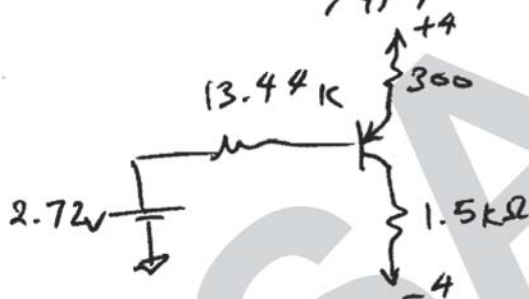
$$I_B = 19.3 \mu\text{A}, I_{BB} = 80 \mu\text{A} \rightarrow I_B \text{ cannot be ignored.}$$



$$4 - 0.7 - 2.72 = I_B (13.44 \text{ k}\Omega + 300 \times 101)$$

$$\rightarrow I_B = 13.3 \mu\text{A} \rightarrow I_C = 1.33 \text{ mA} \quad (7)$$

$$\rightarrow V_C = 1.995 - 4 = -2 \text{ V}$$

$$\rightarrow V_{EC} = 4 - 300 \times 1.33 + 2 = 5.6 \text{ V} \quad (3)$$

(6)

without
part (a)

Name: _____

Student number: _____

Midterm exam

Time: 110 minutes

March 1, 2011


Page: 8/10

Question 4. [30 marks]

The transistor shown in the circuit to the right is operating in its active region. Assume $R_C = 2k\Omega$, $\beta = 100$, and $V_A = \infty$.

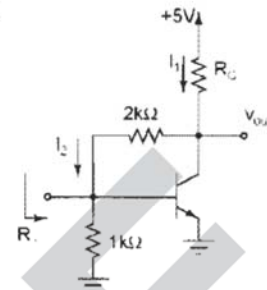4.a. Ignoring I_B , what is the collector voltage of the transistor?

$$V_C = V_{out} = \underline{2.1} \text{ V} \quad \text{(3)}$$



$$I_B = 0 \rightarrow I_2 = \frac{0.7}{1k\Omega} = 0.7\text{mA} \rightarrow V_{out} = 3k \times 0.7 = 2.1\text{V}$$

4.b. What is the collector current of the transistor?

$$I_C = \underline{0.75} \text{ mA} \quad \text{(3)}$$

$$I_1 = \frac{5 - 2.1}{2k} = 1.45\text{mA} \rightarrow I_C = 0.75\text{mA}$$

4.c. Calculate the small signal parameters g_m and r_π .

$$g_m = \underline{30\text{ mS}} \quad \text{(2)} \quad r_\pi = \underline{3.3k} \Omega \quad \text{(2)}$$

$$g_m = \frac{0.75}{25} = 30\text{ mS}$$

$$r_\pi = \frac{100}{0.3 \times 10^{-3}} = 3.3k\Omega$$

Name: _____

Student number: _____


Midterm exam

Time: 110 minutes

March 1, 2011

Page: 9/10

4.d. Draw the small signal equivalent of the circuit.

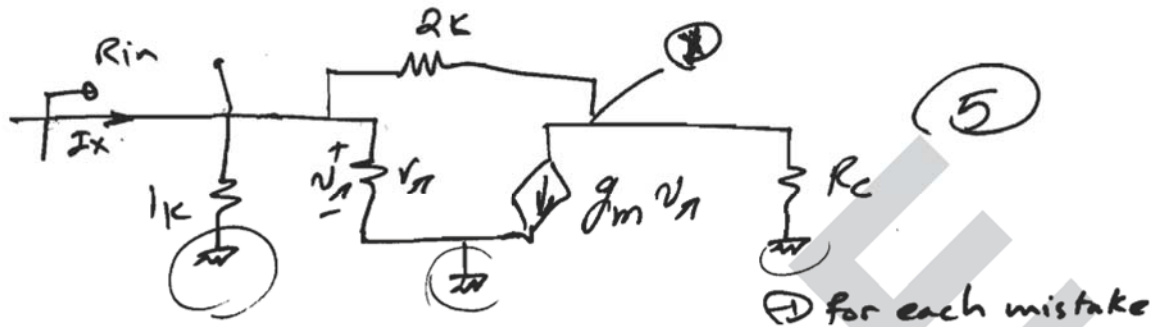4.e. What is the input resistance of the circuit (R_{in} on the graph)?

$$R_{in} = \underline{\underline{60.4 \Omega}}$$

$$\frac{v_x}{1k} + \frac{v_x}{r_{gs}} + \frac{v_x - v_y}{2k} = i_x$$

$$\frac{v_y}{R_L} + \frac{v_y - v_x}{2k} + g_m v_x = 0 \rightarrow$$

$$v_y \left(\frac{1}{R_L} + \frac{1}{2k} \right) = v_x \left(\frac{1}{2k} - g_m \right)$$

$$\rightarrow v_y = \underline{\underline{-29.5 v_x}}$$

$$\rightarrow i_x = v_x \left(\frac{1}{1k} + \frac{1}{3.3k} + \frac{30.5}{2k} \right) \rightarrow$$

$$R_{in} = \frac{v_x}{i_x} = \underline{\underline{60.4 \Omega}} \quad (5)$$